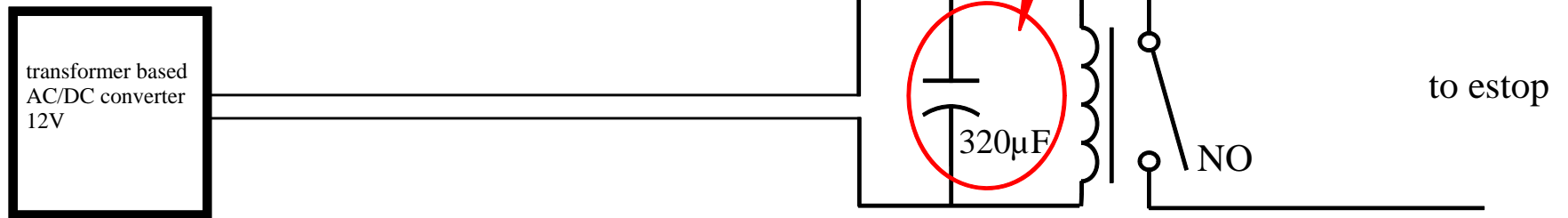


Plug transformer into
surge protected outlet only



How it works:

The transformer holds the relay coil charged and the normally open switch latched (closed), when power is lost to the transformer the relay will release the switch creating an open in the estop circuit causing Mach3 to stop. .