
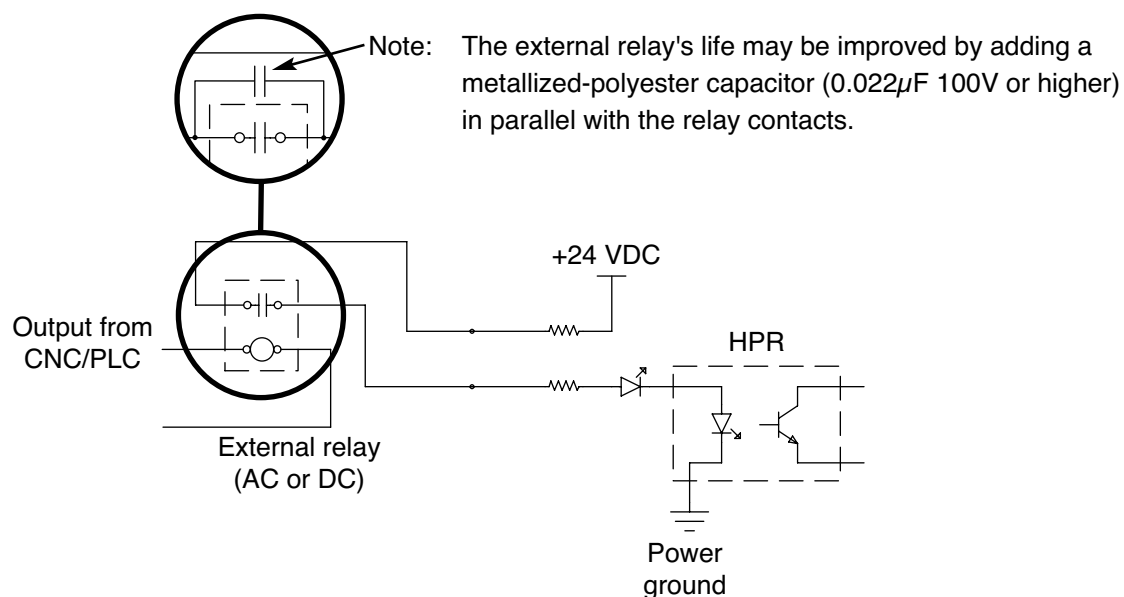


## Examples of input circuits

### 1. Relay interface

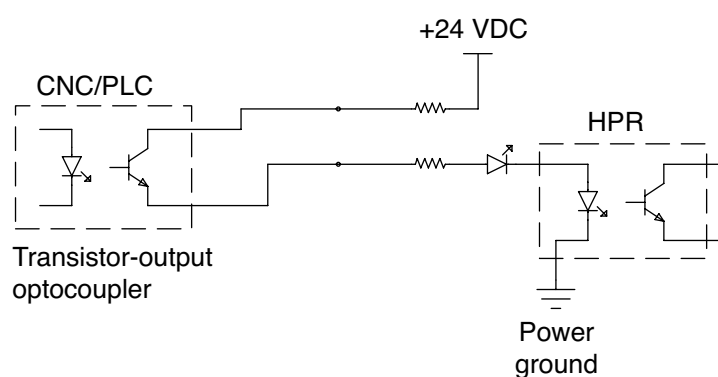

### 2. Optocoupler interface



### 3. Amplified-output interface

